

# FLASH OR PARALLEL TYPE ADC

- It is used to convert analog signal into digital signal
- If we convert n-bit data in a single clock pulse and faster operation.

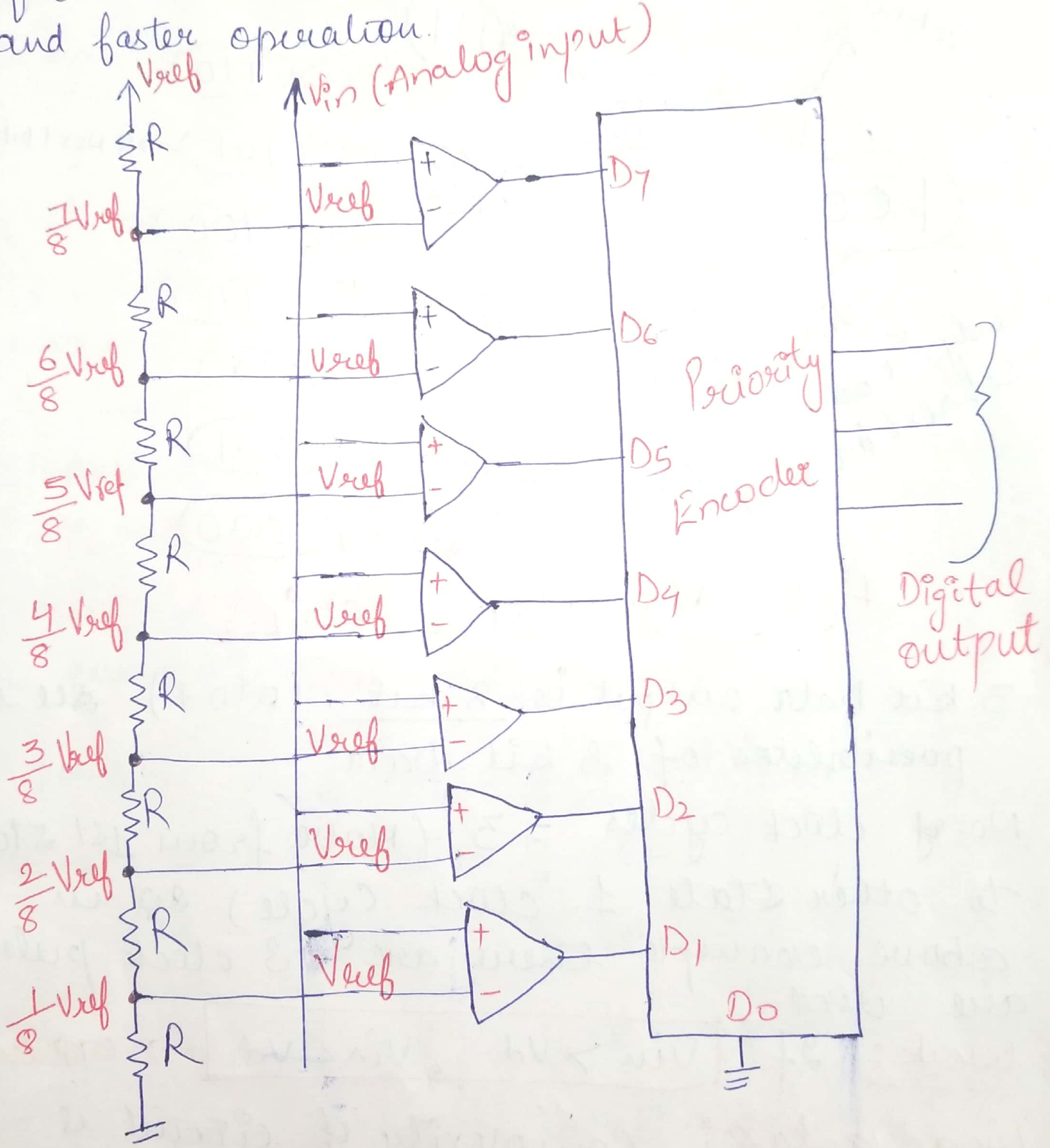


Figure: Parallel type ADC

•  $V_{in}$  = Analog input

Example: Design 3-bit number.

Resistors Required =  $2^n$  resistors =  $2^3 = 8$  Resistors

Comparator Required =  $2^{n-1}$  comparator (OP-AMP)  
=  $2^{3-1} = 2^2 = 4$  comp.

$V_{ref}$  = Reference voltage at -ve terminal of OP-AMP

• This ref. vltg is divided into all the terminals.  
means  $2^{n-1}$  branches

• If  $V_{in} > V_{ref}$  at particular point then your OP-AMP voltage is going to 1 otherwise its zero

$V_{in} > V_{ref}$  OPAMP OIP = High (1)

$V_{in} < V_{ref}$  OPAMP OIP = Low (0)

For example:  $V_{ref} = 8V$ ,  $V_{in} = 8V$ .

1st point D<sub>7</sub>  $\frac{7}{8} V_{ref} = \frac{7}{8} \times 8 = 7V$

D<sub>6</sub>  $\frac{6}{8} V_{ref} = \frac{6}{8} \times 8 = 6V$

D<sub>5</sub>  $\frac{5}{8} V_{ref} = \frac{5}{8} \times 8 = 5V$

D<sub>4</sub>  $\frac{4}{8} V_{ref} = \frac{4}{8} \times 8 = 4V$

D<sub>3</sub>  $\frac{3}{8} V_{ref} = \frac{3}{8} \times 8 = 3V$

D<sub>2</sub>  $\frac{2}{8} V_{ref} = \frac{2}{8} \times 8 = 2V$



Input voltage  $V_{in} = 8V$  so each and every point  
Input voltage is greater than  $V_{ref}$

$$V_{in} > V_{ref} \text{ (each point)}$$

output of OPAMP is always 1.

So you get output of OPAMP = 1

$$D_1 \text{ to } D_7 = 1, \quad D_0 = 0 \text{ (Ground)}$$

Priority Encoder: 8 to 3 Encoder means

Eight input and 3 output.

Structure of Priority Encoder is Ex-OR gate and some diodes internally connected according to that value.

it convert into 8 bit to 3 bit data; so finally we get our digital output data here.

Q1: How many comparators you are required in flash type ADC?  $2^n - 1$

Q2: How many resistors are you required?  $2^n$

Q3: How many clock pulse are required?   
 on - Parallel work.

Q4: Fast ADC among all ADC?

Q5: Disadvantage: complex circuit (Design)